



$i = ?$

If you connect points A and B with an ideal wire, the current in this wire will be I . If you measure the voltage between A and B without connecting them you will obtain voltage U . What will be the current through a resistor R , connecting points A and B? Only I , U and R are known. All the resistors are different.