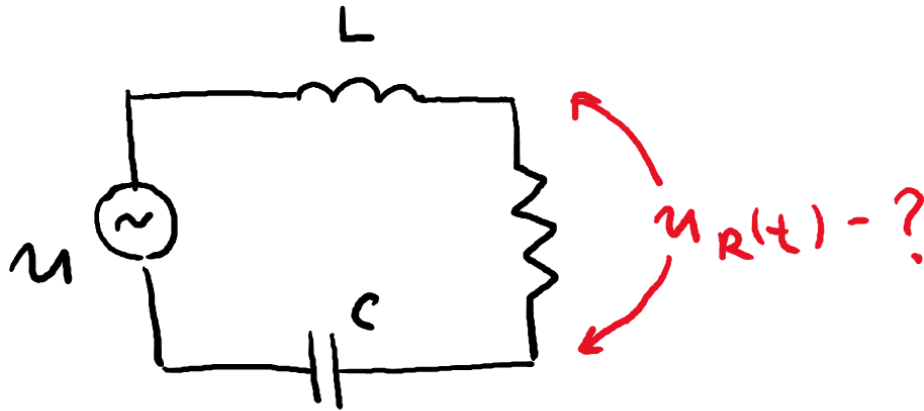


### Homework 9.

We discussed how to use complex numbers to solve AC current circuits. We found that voltage at the inductor is  $V_L = L \frac{dI}{dt}$ , where  $L$  is the inductance and  $I$  – current through the inductor; current through the capacitor is  $I_C = C \frac{dV}{dt}$ , where  $C$  is the capacitance and  $V$  is the voltage at the capacitor. Take a look at the circuit below and try to find the voltage at the resistor as a function of time.



$$\mathcal{U} = \mathcal{U}_0 \cos(\omega t)$$