

# Power (reminder)

- **Power** is the rate of doing work.
- The SI **unit of power** is the watt (W), which is equal to one joule per second  $1W=1J/sec$ .
- Power is a **scalar** quantity (number). It does not have a direction.
- Work may be mechanical work, or **work done by a battery** driving an electric current.
- **Work** can be replaced by **Heat**. That will be **thermal power** rather than mechanical or electric one.

$$P = \frac{W}{t}$$

$$power = \frac{work}{time}$$

## Example:

The power 100 W approximately corresponds to:

- lifting 10 kg to the height of 1 meter in 1 second
- the power required to operate a 100 W bulb
- heating 1 L of water by 15 degree Celsius in 10 minutes


# Power in electric circuits

Ohm's Law

$$V = I \cdot R$$

**V** is **Voltage Drop**, the **Potential Difference** between two ends of a wire (or resistor, light bulb etc). **V** is the difference of electric potential energies of a unit charge between two points.

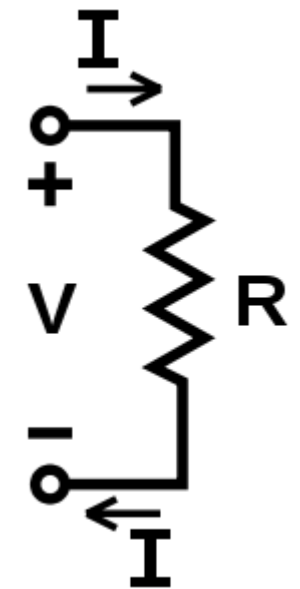- Assume that a battery pushes the charge  $Q$  through the potential difference  $V$  in time  $t$ .
- This means that the work done by battery is  $W=QV$
- The power required for this is  $P=W/t =QV/t=V(Q/t)$
- $Q/t$  can be recognized as the current  $I$
- We have the formula for the electric power  $P=V I$
- Other forms can be obtained using Ohm's law



$$P = I \cdot V$$

*Power = Current × Voltage*

$$P = I \cdot V = I^2 R = \frac{V^2}{R}$$

# Homework

## Problem 1

An electric motor is used to lift a mass  $m=50$  kg to height  $h=10$ m, over time  $t=10$ s. Find the power of the motor and current that runs through it, if the voltage on the motor is  $V=110$ V.

## Problem 2

Find the total power supplied by the battery in circuits shown in the Figure. In both cases the values of all resistances are  $100\ \Omega$  and the voltage produced by battery is  $V_{\text{batt}}=15$  V.

